

Unit 12B – Electrodynamics

- **Current, Voltage and Power**
- **Ohm's Law and Resistance**
- **Simple Circuits**

Competencies

The student will be able to:

- define voltage J/C and power J/s.
- define the current and then define the resistance from the Ohm's Law $V = IR$.
- use Ohm's Law to solve simple circuits and well as series and parallel circuits.
- compute the amount of energy dissipated by a resistor over a given interval of time
- use the law of conservation of energy

Current

Current:

Flow of charge (Charge per time)


$$I = \frac{\Delta Q}{\Delta t}$$

SI-Unit:


Ampere [A], [A]=[C/s]

Direction of Current:

Technical + → -
Electrons - → +

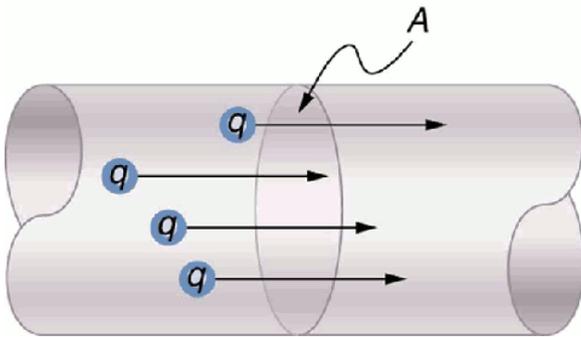


[1]

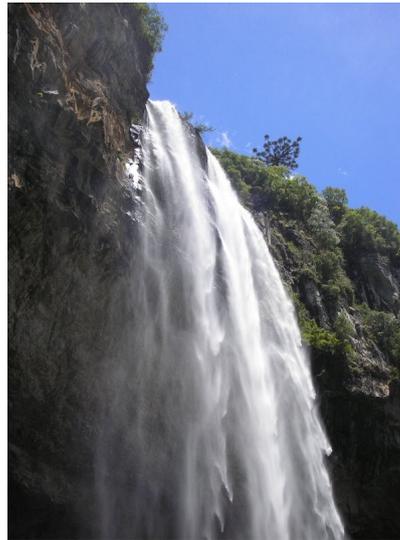

[2]

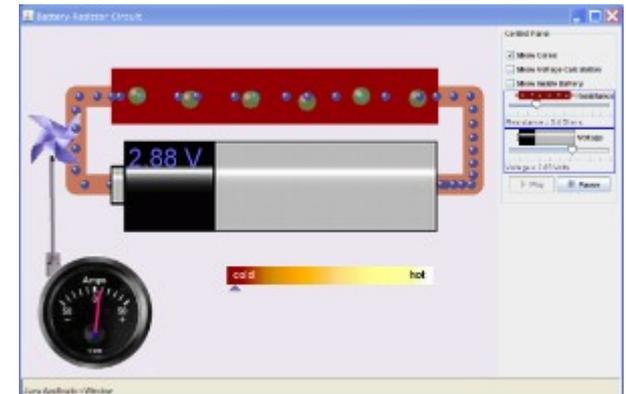Phet-Simulation: Battery Resistor Circuit
<http://phet.colorado.edu/en/simulation/legacy/battery-resistor-circuit>



- [1] **OpenStax, College Physics. OpenStax CNX. April 21, 2016**
<http://cnx.org/contents/Ax2o07Ul@9.31:3ct4v3c5@4/Current>
 Creative Commons 4.0 License <http://creativecommons.org/licenses/by/4.0/>
- [2] Cascata do Caracol, Canela, RS by Stefan Bracher

→ Do Unit XIIB Problem 3-4

Electric Potential (Voltage)

Electric Potential:

Energy per Charge

SI-Unit:

Volts [V], [V]=[J/C]

$$V = \frac{\Delta E}{\Delta Q}$$



Cascata do Caracol, Canela, RS
by Stefan Bracher

Power


Power: Energy per Time

SI-Unit: Watt [W], [W]=[J/s]

$$P = \frac{\Delta E}{\Delta t}$$

$$V = \frac{\Delta E}{\Delta Q}$$

$$I = \frac{\Delta Q}{\Delta t}$$

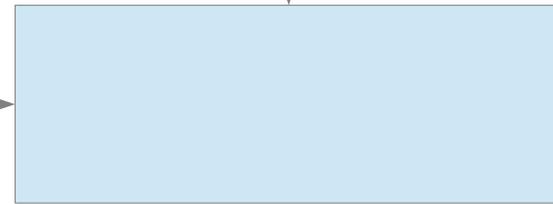

Photos: Cascata do Caracol, Canela, RS
by Stefan Bracher

→ Do Unit XIIB Problem 1, 6-11, 23, 25

Ohm's Law

Ohm's Law: Electric Potential = Resistance times Current

$$V = RI$$

Resistance: $R = V/I$


$$R = V/I$$

SI-Unit: Ohm [Ω], [Ω] = [A/V]

$$I = V/R$$



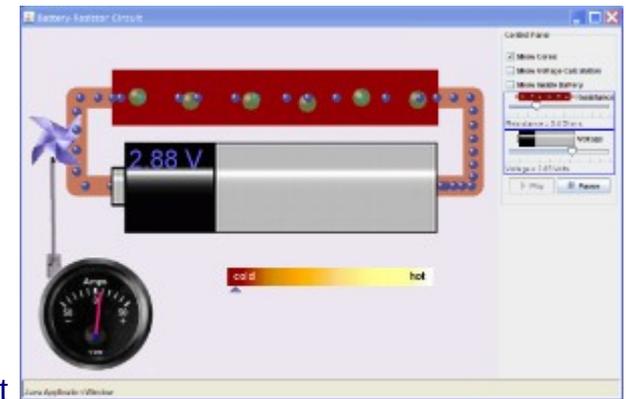"Bangkok traffic jam" by Keng Susumpow
<https://www.flickr.com/photos/kengz/67187556/>
 Creative Commons 2.0 License
<https://creativecommons.org/licenses/by/2.0/>




Phet-Simulation: Battery Resistor Circuit
<http://phet.colorado.edu/en/simulation/legacy/battery-resistor-circuit>

→ Do Unit XIIB Problem 2, 5, 12, 24

Simple Circuits


Series

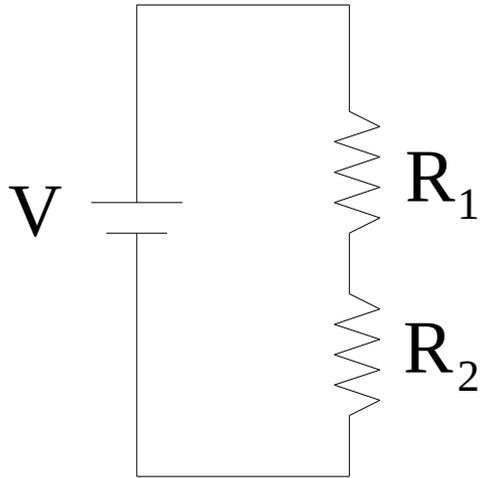

Same current

$$R_{\text{eq}} = R_1 + R_2$$

Parallel

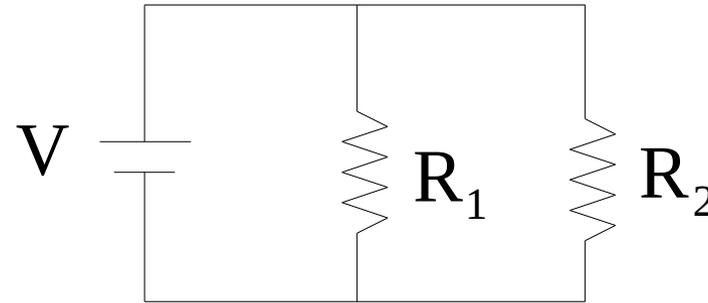

Same Voltage

$$R_{\text{eq}} = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$

→ Do Unit XIIB Problem 13-14

Simple Circuits

Junction Rule: The sum of all currents at a junction is zero
(← Conservation of Charge)

Loop Rule: The sum of all voltages around a closed loop is zero
(← Conservation of Energy)

→ Do Unit XIIB Problem 15-22, 26-29

Additional Resources

- Electric Current, Resistance, and Ohm's Law, OpenStax „College Physics“
http://cnx.org/contents/Ax2o07UI@9.31:En9j99Z_@3/Introduction-to-Electric-Curre
- Circuits and DC Instruments, OpenStax „College Physics“
<http://cnx.org/contents/Ax2o07UI@9.31:E74qWTpP@5/Introduction-to-Circuits-and-D>